 


# Memory Architecture & Interface



Topic 7  
Fall 2019





# Basic of Memory Architecture

- Stores large number of bits

- $m \times n$ :  $m$  rows of  $n$  bits each
- $k = \log_2(m)$  address input signals
- or  $m = 2^k$  rows
- e.g., 4k x 8 memory:  
12 address inputs  
8 data lines

- Memory access

  - r/w**: selects read or write
- enable**: read or write only when asserted







# Basic of Memory Architecture

- Stores large number of bits

- $m \times n$ :  $m$  rows of  $n$  bits each
- $k = \text{Log}_2(m)$  address input signals
- or  $m = 2^k$  rows
- e.g., 4k x 8 memory:  
12 address inputs  
8 data lines

- Memory access

  - r/w**: selects read or write
- enable**: read or write only when asserted



[3]





# Basic of Memory Architecture

- Stores large number of bits

- $m \times n$ :  $m$  rows of  $n$  bits each
- $k = \text{Log}_2(m)$  address input signals
- or  $m = 2^k$  rows
- e.g., 4k x 8 memory:  
12 address inputs  
8 data lines

- Memory access

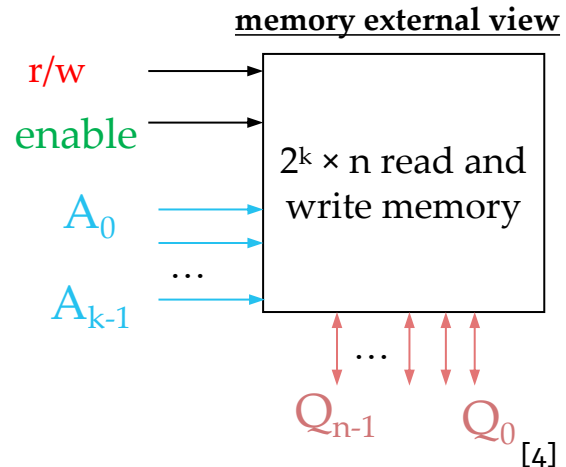 - r/w**: selects read or write
- enable**: read or write only when asserted





# Memory Types

- **Traditional ROM/RAM distinctions**
  - **ROM**  
read only, bits stored without power
  - **RAM**  
read and write, lose stored bits without power
- **Traditional distinctions blurred**
  - Advanced ROMs can be written to  
e.g., **EEPROM**
  - Advanced RAMs can hold bits without power  
e.g., **NVRAM, DDRAM**
- **Write ability**
  - Speed, a memory can be written
- **Storage permanence**
  - ability of memory to hold stored bits after they are written



# Write ability

- **Ranges of write ability**

- **High end**

- processor writes to memory simply and quickly  
e.g., RAM

- **Middle range**

- processor writes to memory, but slower  
e.g., FLASH, EEPROM

- **Lower range**

- special equipment, “programmer”, must be used to  
write to memory

- e.g., EPROM, OTP ROM

- **Low end**

- bits stored only during fabrication  
e.g., Mask-programmed ROM



# Performance

- **Range of storage permanence**
  - **High end**

essentially never loses bits  
e.g., mask-programmed ROM
  - **Middle range**


holds bits days, months, or years after memory's power source turned off  
e.g., NVRAM
  - **Lower range**

holds bits as long as power supplied to memory  
e.g., SRAM
  - **Low end**

begins to lose bits almost immediately after written  
e.g., DRAM



# Performance

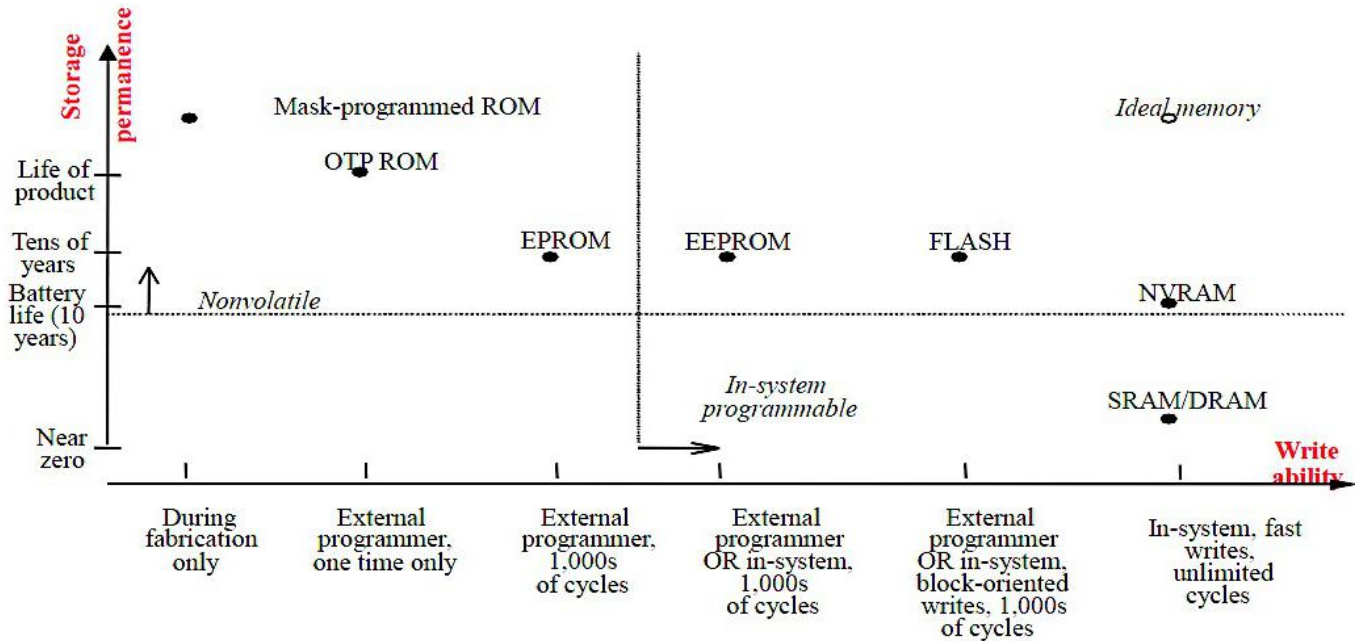

Write ability and storage permanence of memories, showing relative degrees along each axis (not to scale).






# Basic types of RAM

- **SRAM: Static RAM**
  - Memory cell uses flip-flop to store bit
  - Requires 6 transistors
  - Holds data as long as power supplied

## Memory cell internals

 




# Basic types of RAM

- **SRAM: Static RAM**
  - Memory cell uses flip-flop to store bit
  - Requires 6 transistors
  - Holds data as long as power supplied

**SRAM**

Memory cell internals

 



# Basic types of RAM

## ■ SRAM: Static RAM

- Memory cell uses flip-flop to store bit
- Requires 6 transistors
- Holds data as long as power supplied



## ■ DRAM: Dynamic RAM

- Memory cell uses MOS transistor and capacitor to store bit
- More compact than SRAM
- “Refresh” required due to capacitor leak


word's cells refreshed when read

- Typical refresh rate 15.625 microsec.
- **Slower to access than SRAM**

### memory cell internals

  

# Composing memory

 



# Composing memory


- Memory size needed often differs from size of readily available memories
  - Required size **4K x 16** is but available is **2K x 8**
- When **available memory is larger**
  - simply ignore unneeded high-order address bits and higher data lines
- When **available memory is smaller**
  - compose several smaller memories into one larger memory

[13]


 
# Composing memory


- Connect side-by-side to increase width of words




 
# Composing memory


- Connect **side-by-side** to increase width of words




 
# Composing memory

- Connect side-by-side to increase width of words







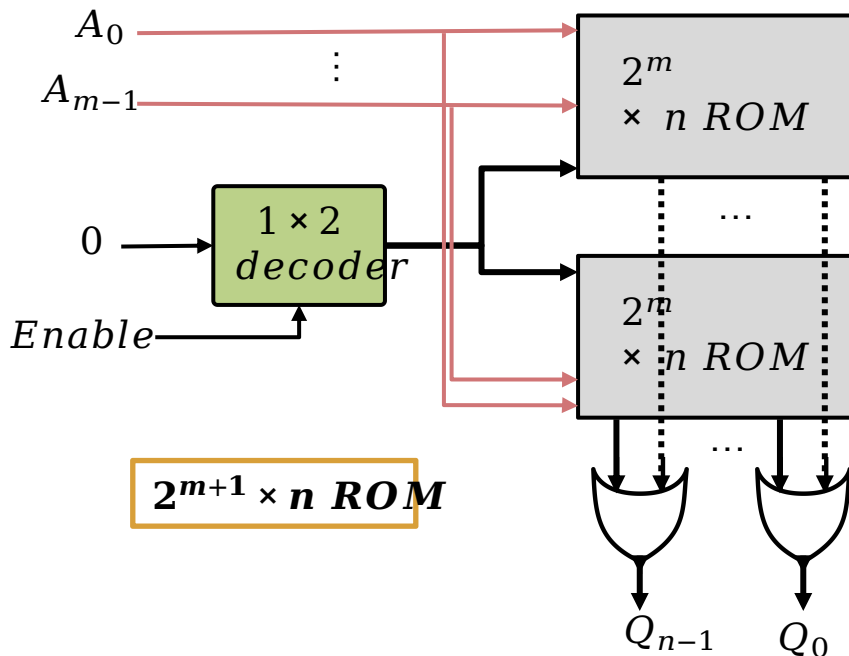
# Composing memory


- Connect **top to bottom** to increase number of words  
Added high-order address line selects smaller memory containing desired word using a decoder




 
# Composing memory: Decoder


- Connect **top to bottom to increase number of words**  
Added high-order address line selects smaller memory containing desired word using a decoder




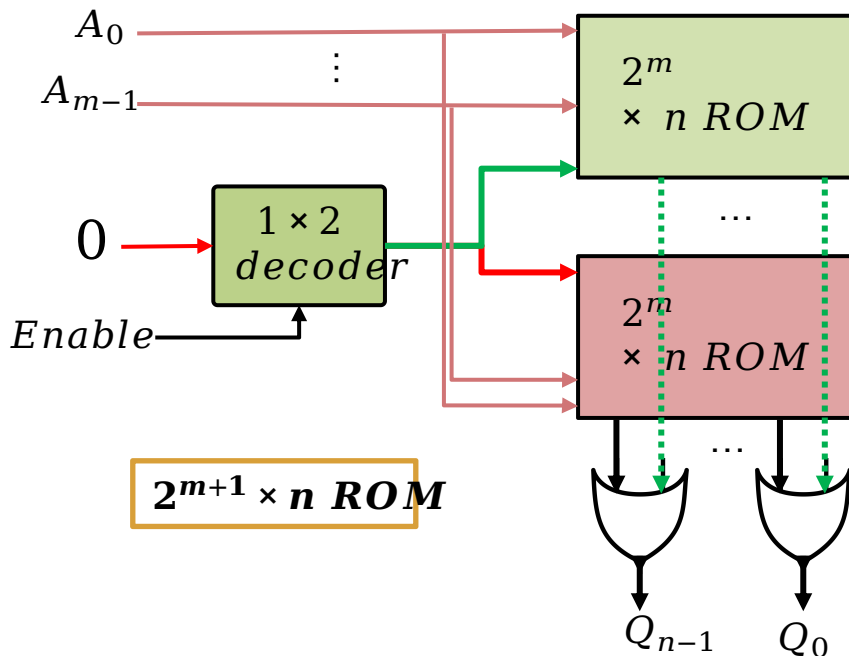
# Composing memory


- Connect **top to bottom** to increase number of words  
Added high-order address line selects smaller memory containing desired word using a decoder




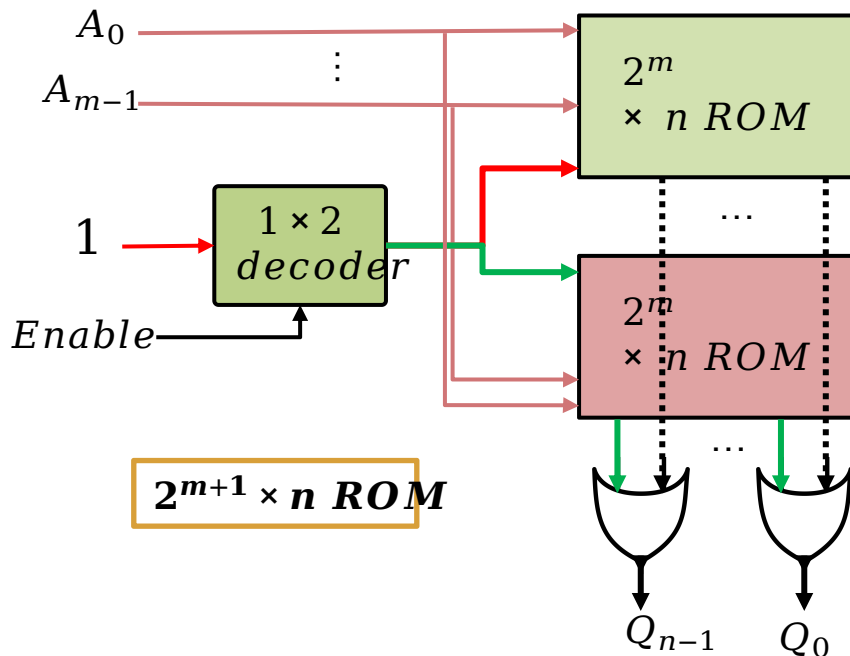
# Composing memory


- Connect **top to bottom** to increase number of words  
Added high-order address line selects smaller memory containing desired word using a decoder




 
# Composing memory

- Combine techniques to increase number and width of words





# Activity


- Compose 1K x 8 ROM into a 2K x 16 ROM





# Activity

- Compose 1K x 8 ROM into a 2K x 16 ROM

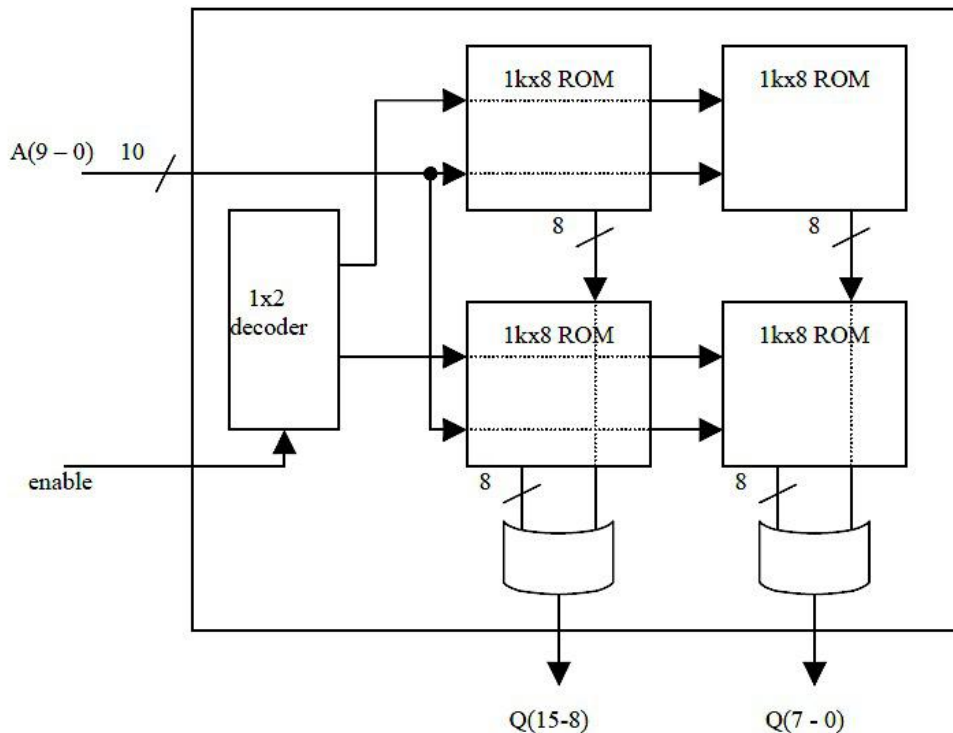




# Interfacing Signals

- Interfacing memory with CPU
  - Address lines
  - Data lines
  - Control lines


Enable, read, write, ready, size etc.

 





# 8088 Minimum Memory Interface

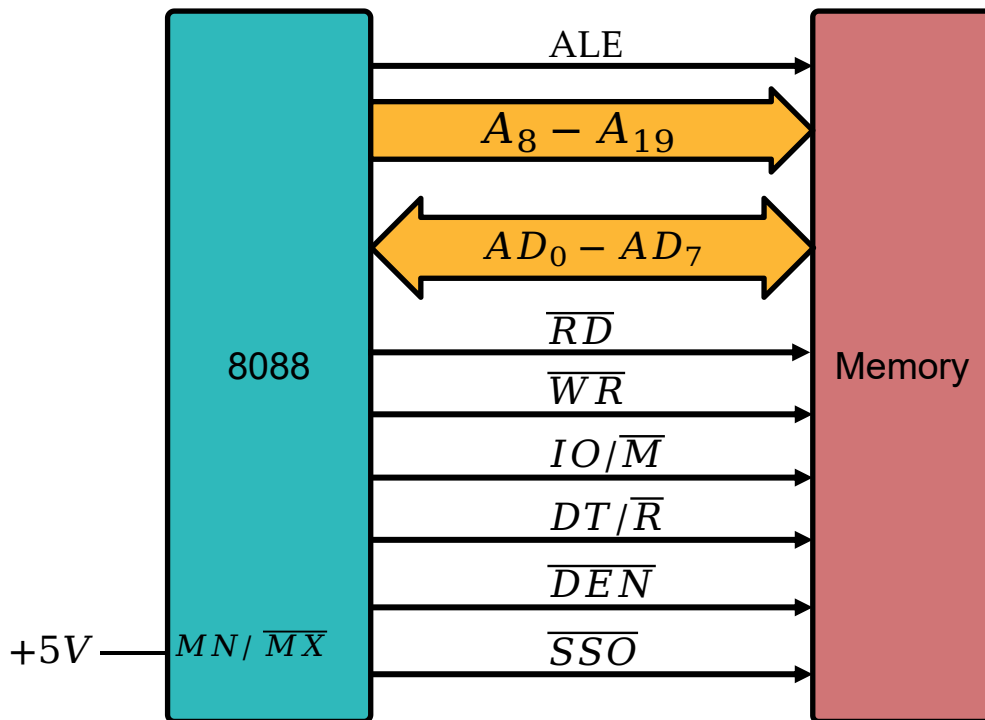

Minimum-mode 8088 memory interface



# Memory Control Signals

**ALE**

**Address Latch Enable** : used to latch the address in external memory

**$IO/\overline{M}$**

**Input-output/Memory** : signal external circuitry whether memory or I/O bus cycle in progress

**$DT/\overline{R}$**

**Data Transmit/Receive** : signal external circuitry whether 8088 is transmitting or receiving data over the bus.

**$\overline{WR}$**

**Write** : identifies a write cycle in progress

**$\overline{RD}$**


**Read** : identifies a read cycle in progress

**$\overline{DEN}$**

**Data Enable** : used to enable data bus.

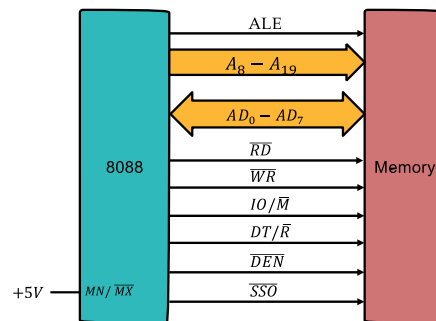**$\overline{SSO}$**


**Status Line** : identifies whether a code or data access is in progress



Minimum-mode 8088 memory interface



# 8088 : Maximum Memory Interface

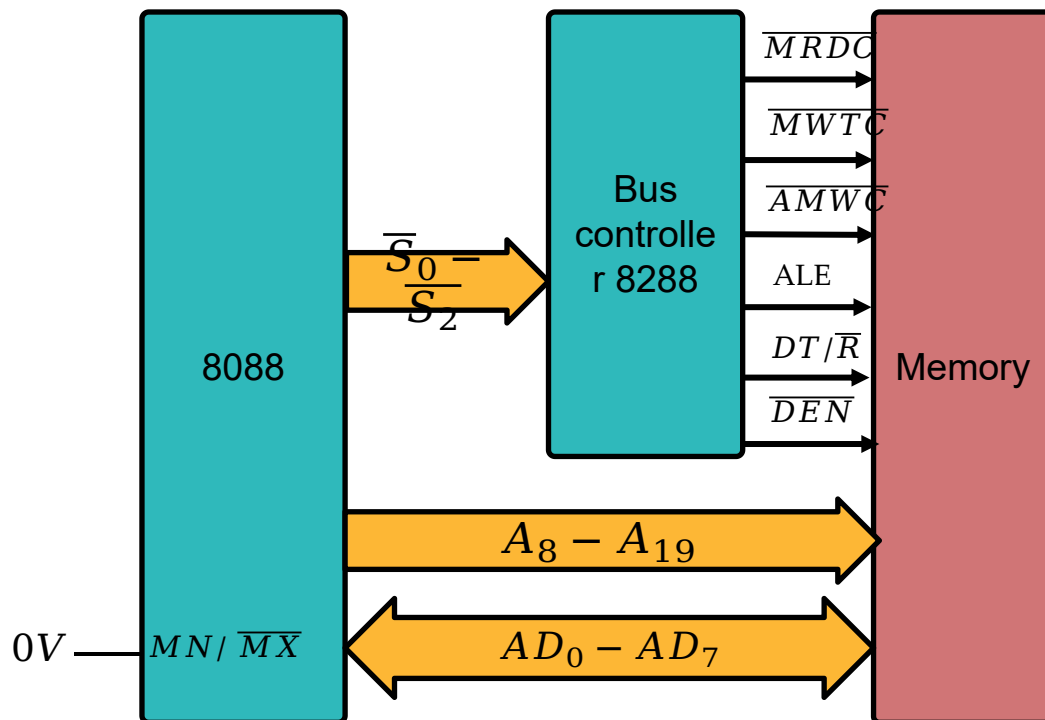

Maximum-mode 8088 memory interface




# Memory control signals

- Maximum Mode Memory Control Signals

**MRDC** – Memory Read Command

**MWTC** – Memory Write Command

**AMWC** – Advanced Memory Write Command

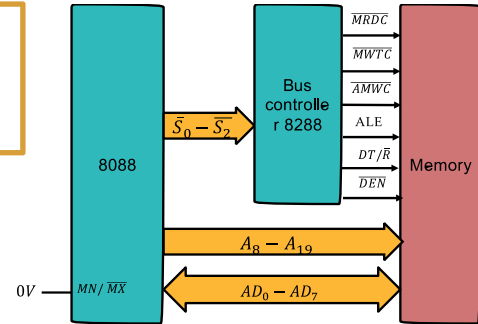


Maximum-mode 8088 memory interface

Status Inputs			CPU Cycle	8288 Command
$\overline{S_2}$	$\overline{S_1}$	$\overline{S_0}$		
0	0	0	Interrupt Acknowledge	$\overline{INTA}$
0	0	1	Read I/O Port	$\overline{IORC}$
0	1	0	Write I/O Port	$\overline{IOWC}$ , $\overline{AIOWC}$
0	1	1	Halt	None
1	0	0	Instruction Fetch	$\overline{MRDC}$
1	0	1	Read Memory	$\overline{MRDC}$
1	1	0	Write Memory	$\overline{MWTC}$ , $\overline{AMWC}$
1	1	1	Passive	None




# 8088 Memory Read Cycle (min. mode)

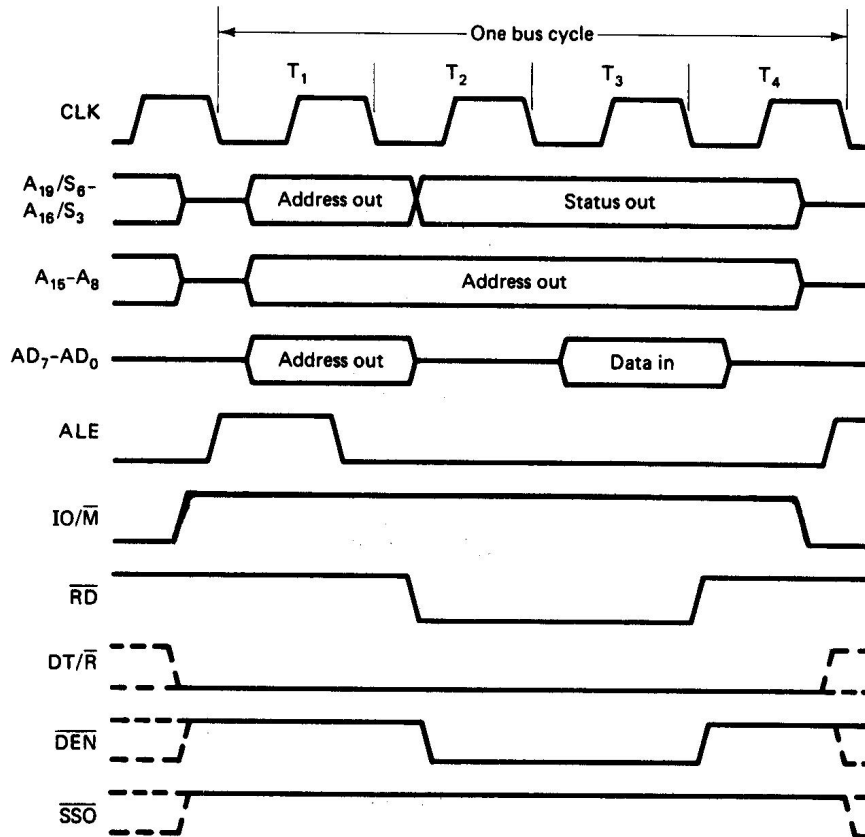



# 8088 Memory Write Cycle (min. mode)

 




# Reading Assignment



- Maximum Mode Read and Write Memory Bus cycles.




# Hardware Organization

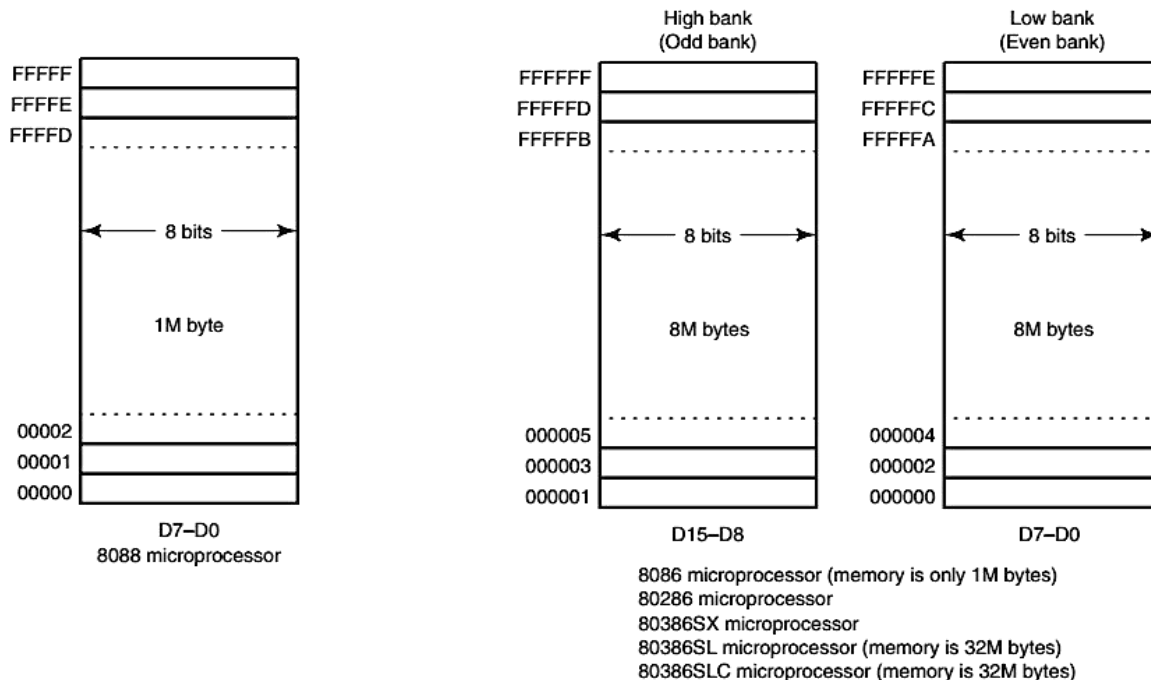






# Hardware Organization

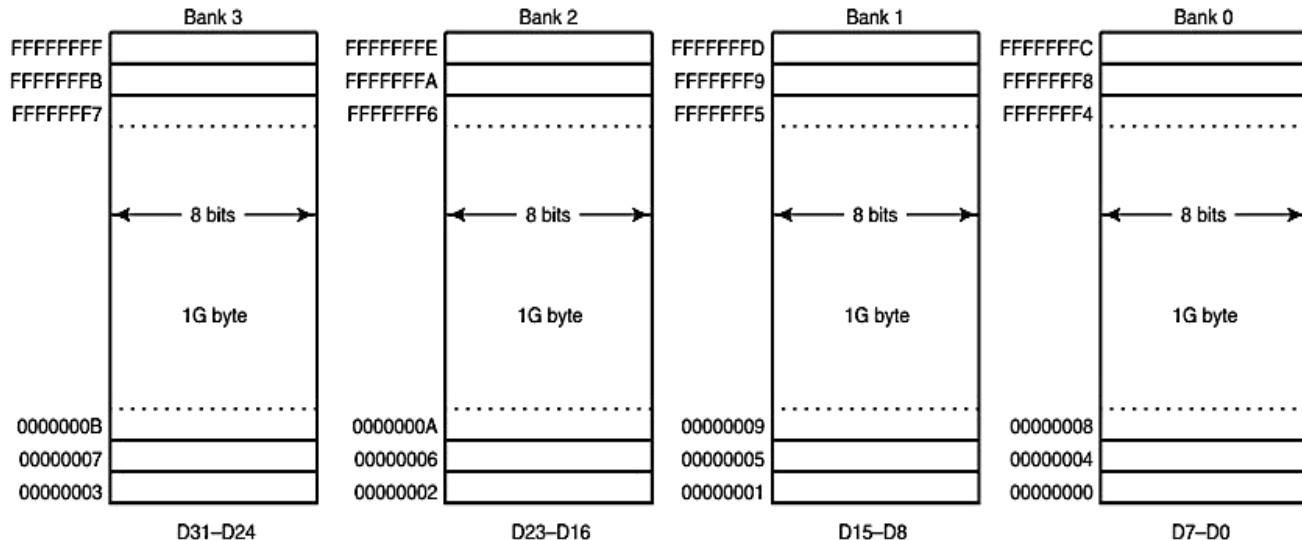

80386DX microprocessor  
80486SX microprocessor  
80486DX microprocessor




# Memory Address Decoding : NAND

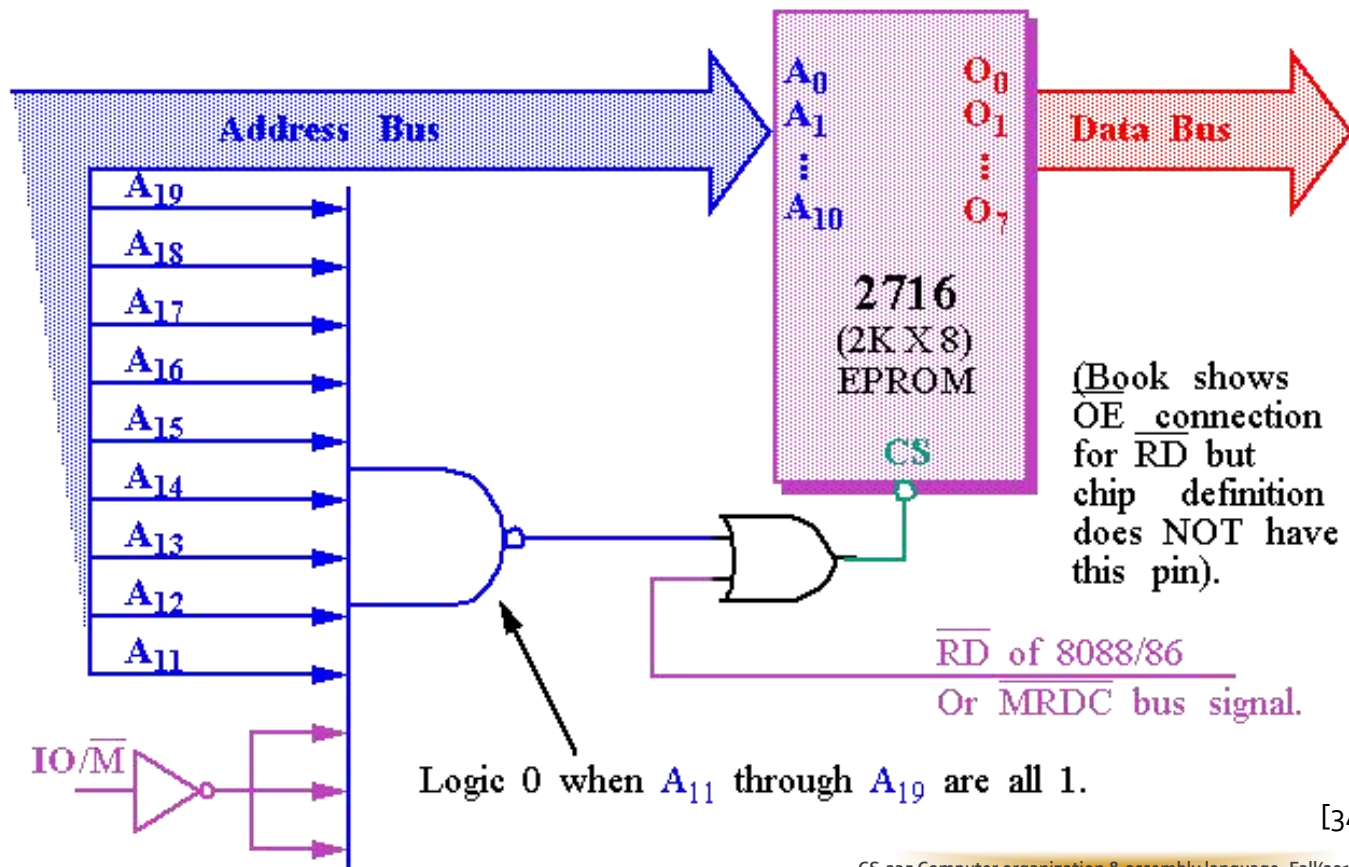




# Memory Address Decoding : 3 to 8

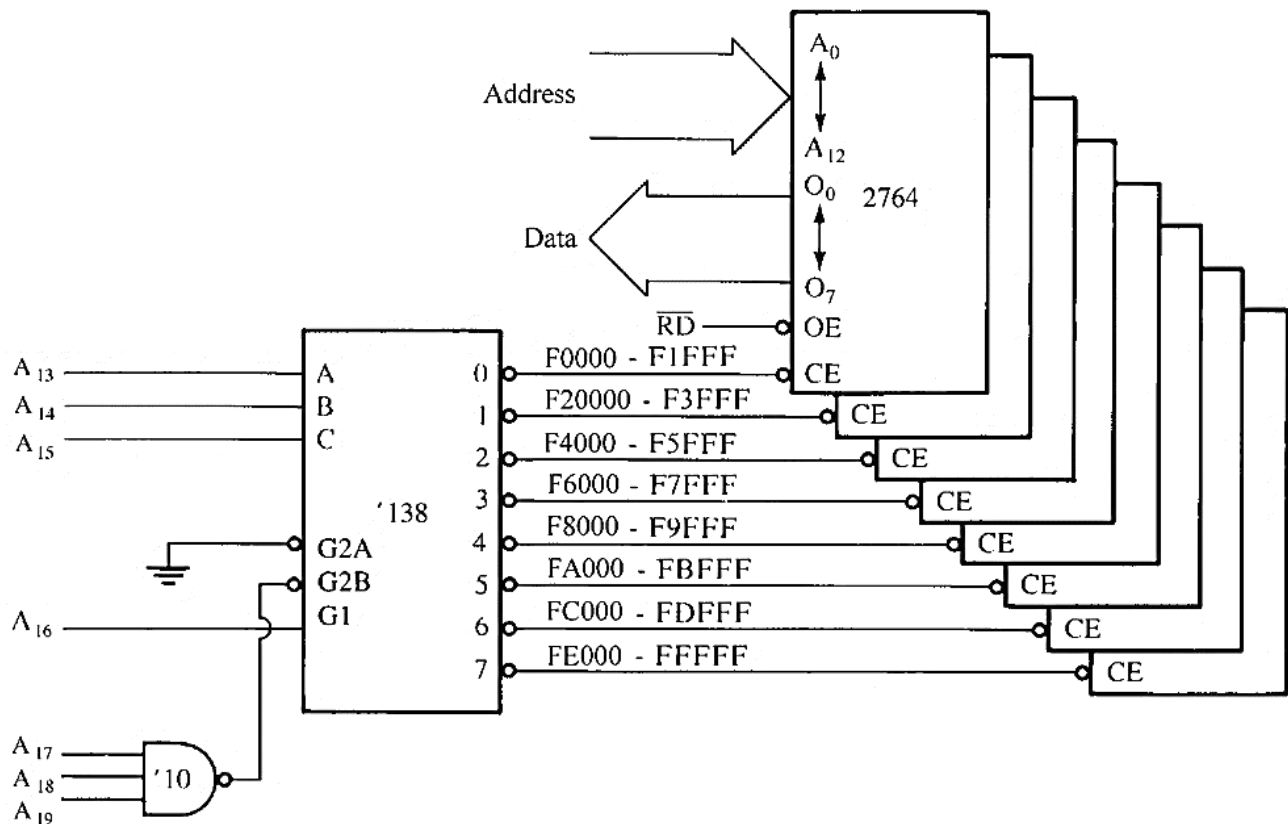




# Memory Address Decoding : 3 to 8

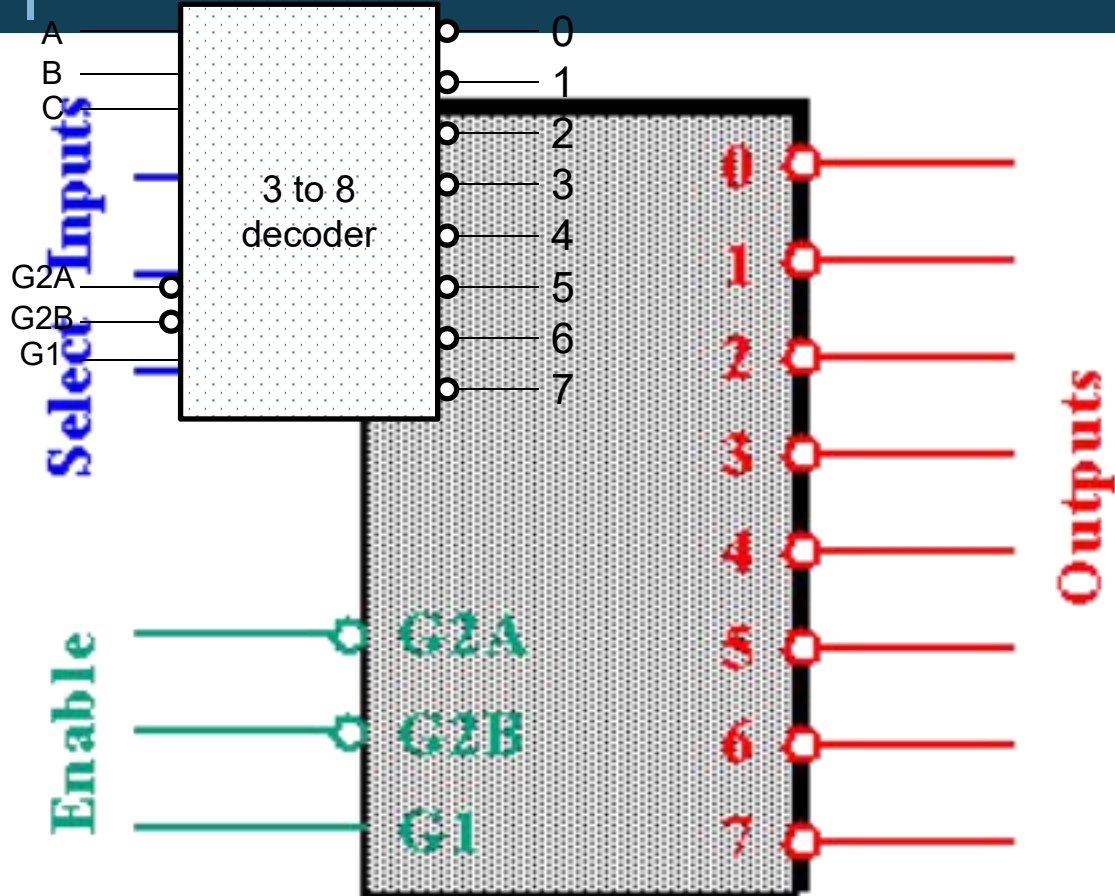



# Memory Address Decoding : 3 to 8

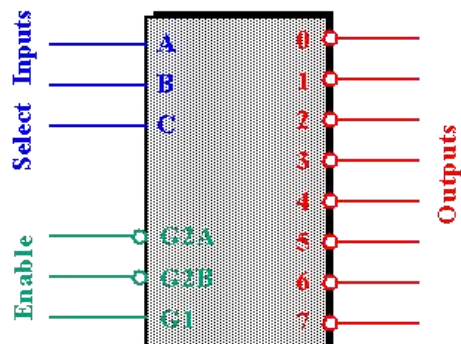


Inputs						Output							
Enable			Select										
G2A	G2B	G1	C	B	A	0	1	2	3	4	5	6	7
1	X	X	X	X	X	1	1	1	1	1	1	1	1
X	1	X	X	X	X	1	1	1	1	1	1	1	1
X	X	0	X	X	X	1	1	1	1	1	1	1	1
0	0	1	0	0	0	0	1	1	1	1	1	1	1
0	0	1	0	0	1	1	0	1	1	1	1	1	1
0	0	1	0	1	0	1	1	0	1	1	1	1	1
0	0	1	0	1	1	1	1	1	0	1	1	1	1
0	0	1	1	0	0	1	1	1	1	0	1	1	1
0	0	1	1	1	0	1	1	1	1	1	0	1	1
0	0	1	1	1	1	1	1	1	1	1	1	0	1

[37]




# Memory Address Decoding : 3 to 8

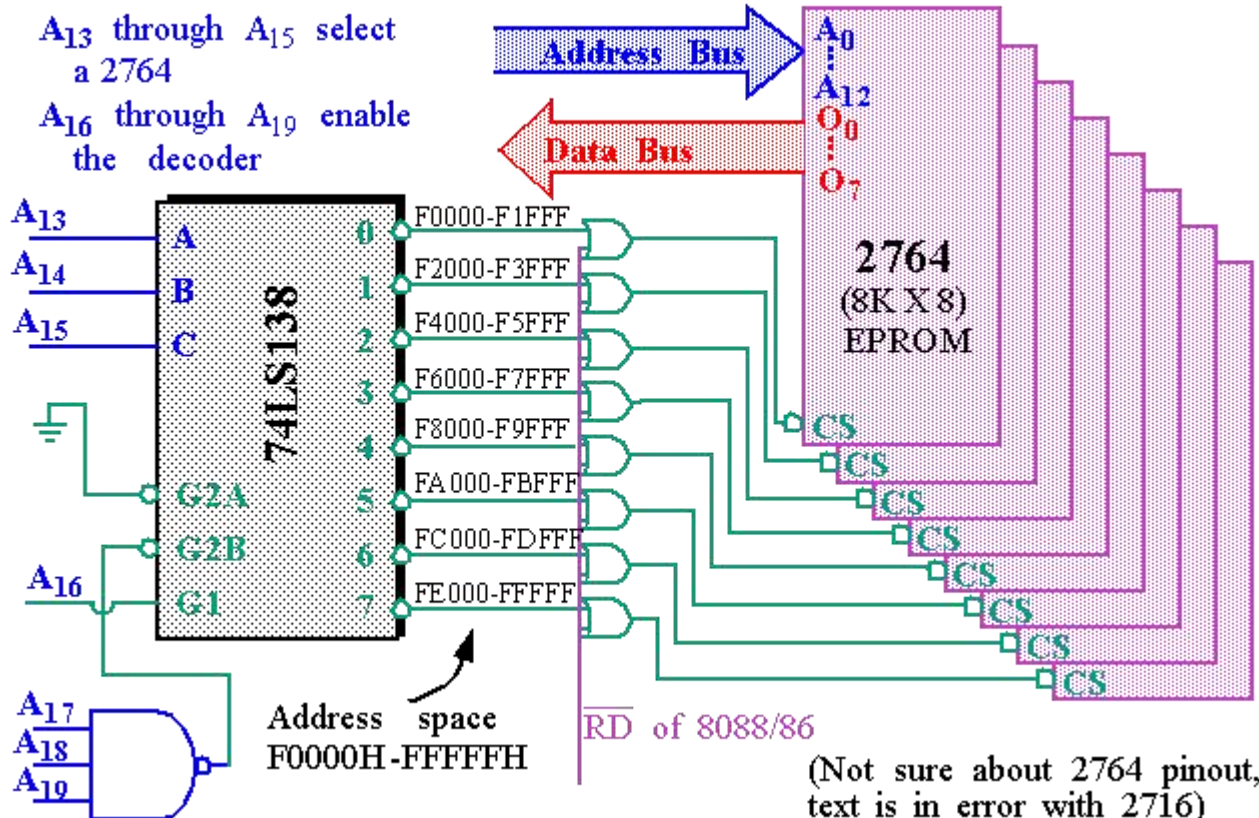





# Memory Interfacing

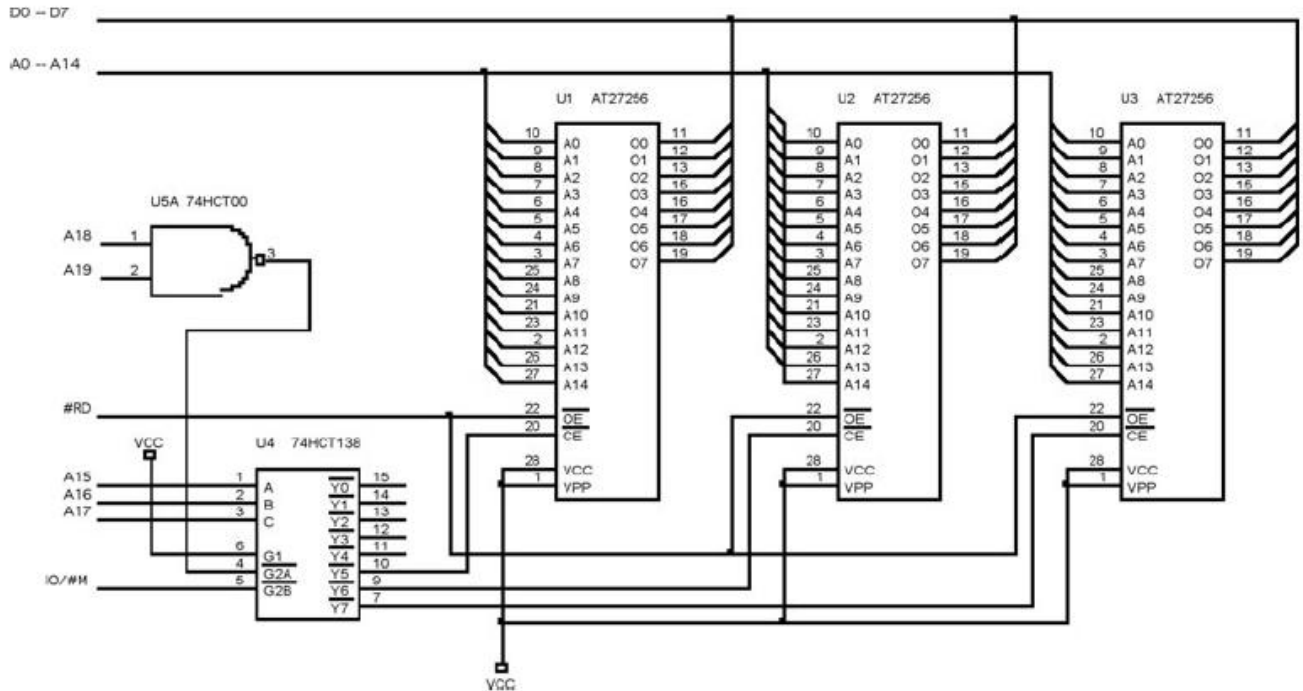

**FIGURE 10-20** Three 27256 EPROMs interfaced to the 8088 microprocessor.



## Method 3

### Programmable Logic Devices (PLDs)

These devices implement a Boolean function against each memory chip connection

- E-g. Programmable Logic Array (PLA)





# HM6264 & 27C256 RAM/ROM devices

- Low-cost low-capacity memory devices
- First two numeric digits indicate device type
  - RAM: 62
  - ROM: 27
- Subsequent digits
  - HM6264 → 8KB (13 address lines, 8 data lines)
  - 27C256 → 32KB (15 address lines, 8 data lines)

**Questions?**

**THANK YOU!**